

Ph 4207, Problem Set #3 (Total Marks 10)
(due 15/04/26)

1. Consider a 3 qubit Gate, $|\psi_1\rangle = |110\rangle$, find each of the quantum states given in the Q-circuit below.

